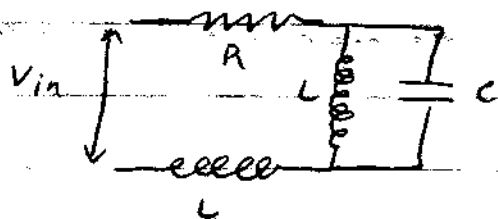


In the ac circuit shown below, the input voltage V_{in} and the circuit elements, R, L, C are known quantities.



(a) Find the frequency $\omega = \omega_{res}$ at which the input impedance $Z_{in} = V_{in}/I_{in}$ is real.

$$Z_R = R; \quad Z_L = i\omega L; \quad Z_C = \frac{-i}{\omega C}$$

Need equivalent Z for $Z_L \parallel Z_C$ part

$$Z_{eq} = \frac{Z_L Z_C}{Z_L + Z_C} = \frac{i\omega L (-i/\omega C)}{i\omega L - \frac{i}{\omega C}} = \frac{L/C}{i(\omega L - \frac{1}{\omega C})} = \frac{-iL}{\omega L - \frac{1}{\omega C}}$$

Then the total equivalent impedance is just

$$Z_{eq} = Z_R + Z_{eq} + Z_L = R + \frac{-iL}{\omega L - \frac{1}{\omega C}} + iL\omega = R + i \left[\frac{\omega L - \frac{1}{\omega C}}{\omega L - \frac{1}{\omega C}} \right]$$

We are told that at $\omega = \omega_{res}$, Z_{eq} is just real (i.e. $= R$), so

$$\frac{\omega L - \frac{1}{\omega C}}{\omega L - \frac{1}{\omega C}} = 0 \Rightarrow \omega L - \frac{1}{\omega C} = 0 \Rightarrow \omega^2 L C - 1 = 1 \Rightarrow \omega^2 = \frac{2}{LC}$$

$$\text{so } \omega_{res} = \omega_x = \sqrt{\frac{2}{LC}}$$

(b) Assuming L and C are ideal (i.e. non-dissipative), then the only loss is due to the resistor:

$$\langle P \rangle = \frac{1}{2} V_0 I_0 \cos \phi \quad \text{where } V_0 \text{ \& } I_0 \text{ are the maximum values of voltage and current.}$$

ϕ is the angle between the voltage and current.

now

$$\phi = \arctan\left(\frac{X}{R}\right) \quad X \text{ is the reactance and } R \text{ is the resistance in } Z = R + iX$$

at $\omega = \omega_{res}$ $X=0$ so $\phi=0$ as well, hence

$$\langle P \rangle = \frac{1}{2} V_0 I_0 \quad \text{or} \quad I_0 = \frac{V_0}{R} \quad \text{or} \quad V_0 = I_0 R$$

in terms of known quantities $\langle P \rangle = \frac{1}{2} \frac{V_0^2}{R}$

but for (d) we will actually use $\langle P \rangle = \frac{1}{2} I_0^2 R$

(c) At $\omega = \omega_{res}$, what is the stored energy, U_{stored} ?

Solving part (d) first and reverse engineering $U_{stored} = \frac{1}{2} L I^2$
as for why that is as opposed to $\frac{1}{2} C V^2$ I don't know.

(d) Find the quality factor $Q = \omega_{res} \frac{U_{stored}}{P_{dissip}}$

From the above two answers:

$$Q = \omega_{res} \frac{\frac{1}{2} L I^2}{\frac{1}{2} I^2 R} = \frac{\omega_{res} L}{R}$$

As for the reverse engineering part, first solve the simpler series R, L, C circuit (see "Basic Electronics for Scientists", B. R. Hopkins, p. 8d)

$$Z_{eq} = Z_R + Z_L + Z_C = R + i[\omega L - \frac{1}{\omega C}]$$

at ω_{res} (where $\omega_{res} = \frac{1}{\sqrt{LC}}$) $Z_{eq} = R + i[\sqrt{\frac{L}{C}} - \sqrt{\frac{L}{C}}] = R$
(which is exactly what we have).

So we can write in general

$$I = \frac{V}{|Z|} = \frac{V}{|R + i(\omega L - \frac{1}{\omega C})|} = \frac{V}{R} \frac{1}{|1 + \frac{i(\omega L - \frac{1}{\omega C})}{R}|} = \frac{V}{R} \frac{1}{(1 + \frac{1}{R^2}(\omega L - \frac{1}{\omega C})^2)^{1/2}}$$

$$\text{as } |R + iX| = \sqrt{R^2 + X^2}$$

↑ ↑
resistive reactive

which can also be written as:

$$I = \frac{V}{R} \frac{1}{(1 + \underbrace{(\frac{\omega L - \frac{1}{\omega C}}{R})^2}_{\equiv Q^2})^{1/2}}$$


We can do a similar thing in our case:

$$I = \frac{V}{|Z|} = \frac{V}{|R + i(\omega L - \frac{1}{\omega C} - \omega_0 L)|} = \frac{V}{R} \frac{1}{|1 + \frac{i}{R}(\omega L - \frac{1}{\omega C} - \omega_0 L)|}$$

$$= \frac{V}{R} \frac{1}{(1 + \underbrace{(\frac{\omega L - \frac{1}{\omega C} - \omega_0 L}{R})^2}_{\equiv Q^2})^{1/2}}$$

$$\text{Check } \omega = \omega_{res}: \frac{V}{R} \frac{1}{(1 + Q^2[1 - \frac{1}{Q^2}]^2)^{1/2}} = \frac{V}{R} \frac{1}{(1 + Q^2[1 - 1])^{1/2}} = \frac{V}{R} \checkmark$$

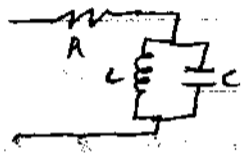Note: If the series inductance were removed



then this circuit would have an infinite impedance at wires and no current would flow! Amazing, what a simple inductor in the right place can do.