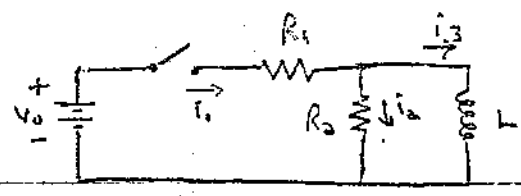


a)
Fall 1999
#5



$V_0 = 100\text{V}$
 $R_1 = 10\ \Omega$
 $R_2 = 100\ \Omega$
 $L = 10\text{H}$

(i) at $t=0$ switch is closed. Find total energy dissipated in R_2 using the loop rule on the smaller loop yields

$$V_0 - i_1 R_1 - i_2 R_2 = 0 \Rightarrow i_1 = \frac{V_0 - i_2 R_2}{R_1}$$

for the larger loop, recall the voltage drop across an inductor is given by $V_L = L \frac{di}{dt}$
Thus the loop rule yields:

$$V_0 - i_1 R_1 - L \frac{d}{dt}(i_1 - i_2) = 0$$

$\underbrace{i_1 - i_2}_{= i_2}$

$$\cancel{V_0} - \cancel{V_0} + i_2 R_2 - L \frac{d}{dt} \left(\frac{V_0 - i_2 R_2}{R_1} - i_2 \right) = 0$$

$$L \frac{d}{dt} \left(i_2 \left(\frac{R_2}{R_1} + 1 \right) \right) = -i_2 R_2$$

$$L \left(\frac{R_2 + R_1}{R_1} \right) \frac{di_2}{dt} = -i_2 R_2 \Rightarrow \frac{di_2}{dt} = \frac{-i_2 R_2 R_1}{L(R_2 + R_1)}$$

$$\frac{di_2}{i_2} = \frac{-R_2 R_1}{L(R_2 + R_1)} dt$$

$$\ln i_2 = \frac{-R_2 R_1 t}{L(R_2 + R_1)} + \text{const} \Rightarrow i_2 = C \exp\left(\frac{-R_2 R_1 t}{L(R_2 + R_1)}\right)$$

at $t=0$ all current flows through resistors, thus $i_2(0) = \frac{V_0}{R_1 + R_2}$

$$i_2(t) = \left(\frac{V_0}{R_1 + R_2} \right) \exp\left(\frac{-R_2 R_1 t}{L(R_2 + R_1)}\right)$$

Energy dissipated given by $i^2 R$

$$W = \int_0^{\infty} i_2^2 R_2 = \frac{V_0^2 R_2}{(R_1 + R_2)^2} \int_0^{\infty} e^{-2\alpha t} dt = \frac{V_0^2 R_2}{(R_1 + R_2)^2} \left(\frac{-1}{2\alpha} \right) \left[e^{-2\alpha t} \right]_0^{\infty}$$

$= \frac{1}{2\alpha} = 17$

$$W = \frac{V_0^2 R_2 L (R_2 + R_1)}{2(R_2 + R_1)^2 R_2 R_1} = \boxed{\frac{L V_0^2}{2 R_1 (R_2 + R_1)} = W}$$

ii) after opening switch, the loop rule gives $L \frac{di}{dt} + i R_2 = 0$

$$\frac{di}{dt} = -\frac{i R_2}{L} \Rightarrow i = C e^{-\frac{R_2 t}{L}}$$

at t_0 , $i = \frac{V}{R_1}$, thus


$$i(t) = \frac{V}{R_1} e^{-\frac{R_2 t}{L}}$$

the power dissipated is thus

$$W = \int_0^{\infty} \left(\frac{V_0}{R_1}\right)^2 R_2 e^{-\frac{2R_2 t}{L}} dt = \frac{V_0^2}{R_1^2} R_2 \left(\frac{L}{2R_2}\right) \left[e^{-\frac{2R_2 t}{L}}\right]_0^{\infty}$$

$$\boxed{W = \frac{V_0^2 L}{2 R_1^2}}$$

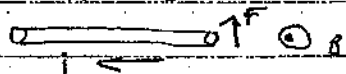b) Can a copper wire be levitated in Earth's magnetic field



$$F = i dL \times \vec{B} \Rightarrow i L B = mg = \rho_m K A g$$

$$\rho_m g = \frac{i B}{A} = j B$$

use $j = i/A$
Current density

$$j = \frac{\rho_m g}{B} \Rightarrow i = \frac{\rho_m g A}{B}$$

$$\text{Power} = i^2 R$$

$$= \left(\frac{\rho_m g A}{B}\right)^2 \frac{\rho_e L}{A}$$

$$R = \frac{\rho_e L}{A}$$

$$= \frac{\rho_m \rho_e g^2}{B^2} (AL)$$

$\underbrace{AL}_{=V}$

$$\boxed{\frac{\text{Power}}{\text{Volume}} = \frac{\rho_m \rho_e g^2}{B^2}}$$