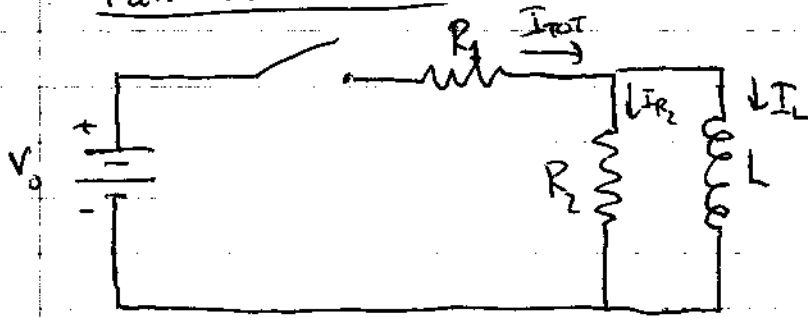


①


Fall '99 #5



Given:  
 $V_0 = 100V$ ,  
 $L = 10H$ ,  
 $R_1 = 10\Omega$ ,  $R_2 = 100\Omega$

we know  $V_L = -L \frac{dI}{dt}$ ,  $V_R = IR$

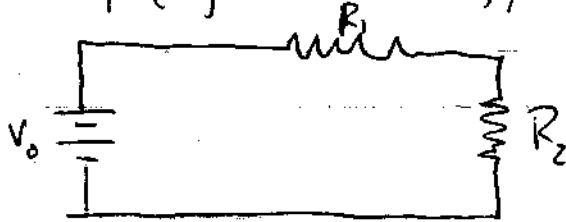
i) Initially (right after  $t=0$ ), system like:



L resists  $\Delta I$

$$\Rightarrow I_{R_2}(0) = \frac{V_0}{R_1 + R_2}$$

Eventually though, after long time:

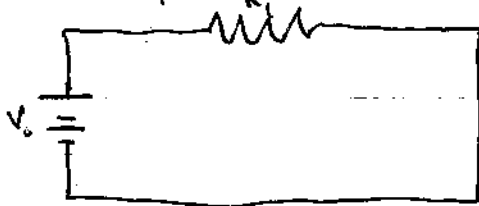

$$\Rightarrow I_{R_2}(\infty) = 0$$

In general, for any electrical component  $P=IV$ , for resistor here

$$P = I_{R_2}^2 R_2 \Rightarrow \text{find } I_{R_2}(t)$$

From kirchoff's Laws; we can look @ sub-loops:

$$V_0 - I_{tot} R_1 - I_{R_2} R_2 = 0 \quad \text{\#1}$$

$$V_0 - I_{tot} R_1 - L \frac{dI_L}{dt} = 0 \quad \text{\#2}$$

\#1  $\rightarrow$  \#2:

$$V_0 - V_0 + I_{R_2} R_2 - L \frac{dI_L}{dt} = 0$$

$$I_{R_2} R_2 - L \frac{d}{dt} (I_{tot} - I_{R_2}) = 0$$

(2)

$$\#1 \rightarrow I_{R_2} R_2 - L \frac{d}{dt} \left( \frac{V_0}{R_1} - I_{R_2} \frac{R_2}{R_1} - I_{R_2} \right) = 0$$

$$I_{R_2} R_2 + L \left( \frac{R_2}{R_1} + 1 \right) \frac{d}{dt} I_{R_2} = 0$$

$$\rightarrow \frac{dI_{R_2}}{dt} = -I_{R_2} \left( \frac{R_2 R_1}{L(R_1 + R_2)} \right)$$

• you can assume a form like

$$I_{R_2}(t) \sim e^{-\frac{R_2 R_1}{L(R_1 + R_2)} t}$$

• but we know IC  $I(0) = \frac{V_0}{R_1 + R_2}$ , so

$$I_{R_2}(t) = \frac{V_0}{R_1 + R_2} e^{-\frac{R_2 R_1}{L(R_1 + R_2)} t}$$

• Now,  $P = I_{R_2}(t)^2 R_2$ , so

$$W = \int_0^{\infty} \left( \frac{V_0}{R_1 + R_2} \right)^2 e^{-\frac{2R_2 R_1}{L(R_1 + R_2)} t} \cdot R_2 dt$$


$$= \frac{V_0^2 R_2}{(R_1 + R_2)^2} \cdot \frac{L(R_1 + R_2)}{2R_2 R_1} e^{-\frac{2R_2 R_1}{L(R_1 + R_2)} t} \Bigg|_0^{\infty}$$

$$W = \frac{V_0^2 L}{2(R_2 + R_1)} = 45.5 \text{ J}$$

(c) energy stored in L will all be dissipated by  $R_2$  (assuming as ~~usual~~ usual negligible resistance ~~within~~ within L)

$$W_{R_2} = \frac{1}{2} L I_L^2(0) = \frac{1}{2} L \left( \frac{V_0}{R_1} \right)^2 = 500 \text{ J}$$

3

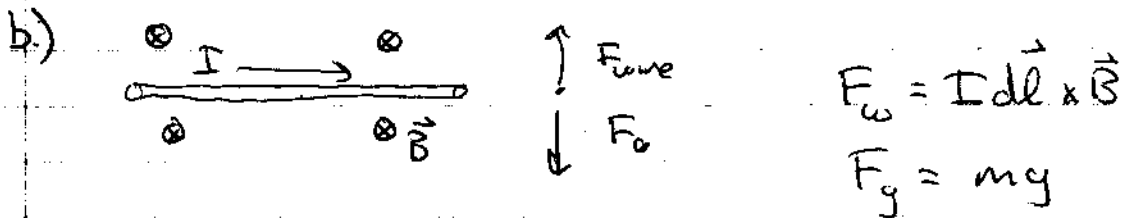

$$ILB = \rho_m V_a g$$

$$\rightarrow I = \frac{\rho_m g A}{B} \quad (\text{know, you want in terms of } I \text{ to get power})$$

$$P = I^2 R = \frac{\rho_m^2 g^2 A^2}{B^2} R \quad \text{but } R = \frac{\rho_e L}{A}, \text{ so}$$

$$P = \frac{\rho_m^2 g^2 A L \rho_e}{B^2}$$

$$\Rightarrow \frac{P}{V} = \frac{\rho_m^2 g^2 \rho_e}{B^2}$$